OHMI TEST ASSIGNMENT: Arduino LED Blink

Use one Arduino Uno, one breadboard, one red LED,

one 220 ohm resistor, and jumper wires.

LED forward voltage: 2 V. Maximum LED current: 20 mA.

Arduino digital pin 9 uses 5 V logic.

Connect D9 through the resistor to LED anode.

Connect LED cathode to Arduino GND.

Program the LED to turn on for 1 second, then off

for 1 second, repeatedly. Explain why the resistor

is in series. Expected result: visible blinking.

This is a fictional assignment, not a tested circuit.